

North South University
Department of Electrical & Computer Engineering
LAB REPORT

Course Code : EEE/ETE 141 L

Course Title: DC Circuit Lab

Course Instructor: Md. Nazmul Bari

Experiment Number: 03

Experiment Name:

Loading Effect of Voltage Divider Circuit.

Date of Experiment: 16/07/2021

Date of Submission: 28/07/2021

Section: 12

Group Number: 04

Submitted By		Score
	Student Name	ID
1.	Khalid Hasan Prodhan	1812188642
2.	Zannatul Ferdous Ananna	1921177042
3.	Nazmoon Nahar Punom	1922049042
4.	Parinda Rahman	1931804042

1.NAME OF THE EXPERIMENT: Loading Effect of Voltage Divider Circuit

Title: Loading Effect of Voltage Divider Circuit.

Objectives:

- To analyze how the voltage divider circuit behaves when there is no load resistance connected
- Evaluate the performance of voltage divider due to the loading

Equipment list:

- Trainer Board
- DMM
- $2 \times 560\Omega$ resistors
- $1 \times (0-10k\Omega)$ variable resistor

4.THEORY:

4. Theory:Loading Effect of Voltage Divider Circuit.

The voltage divider is a circuit used to create a voltage less than or equal to the input voltage. The voltage divider is used only where the voltage is regulated by dropping a particular voltage in a circuit. Most commonly the voltage divider is used in potentiometers.

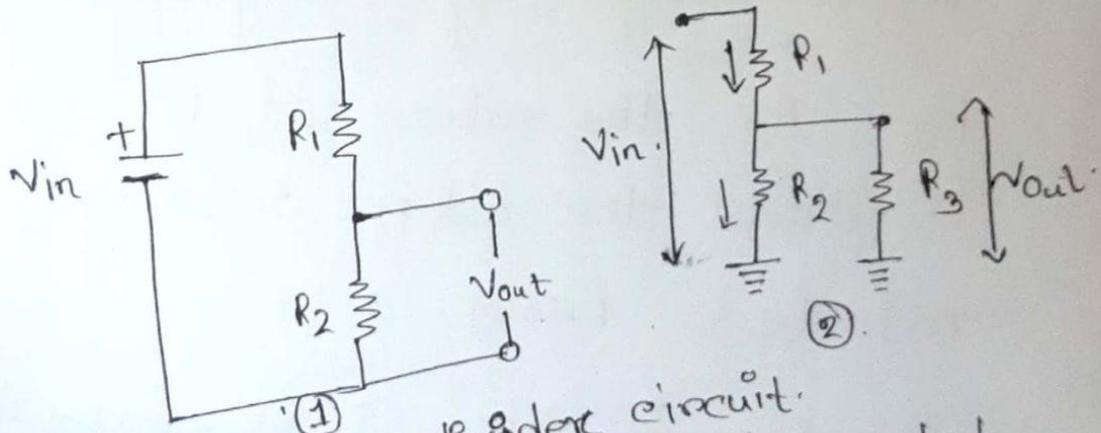


Fig 1: Voltage divider circuit.

Fig 2: Voltage divider with load connected.

Voltage divider circuit provides a simple way to convert a DC voltage to another lower DC voltage.

A voltage divider is basically an electronic circuit network using resistors. In this network resistors are connected in series across the supply voltage, and the output is extracted across one of the resistors for getting the desired equivalent dropped voltage. A potentiometer can also be used to change output voltage by changing the resistance R_2 . As the value of R_2 is changed it allows the output voltage to be adjusted from 0 to V_{in} .


According to Voltage Divider rule :

$$V_{out} = V_{in} \frac{R_2}{R_1 + R_2} \quad (1)$$


When we have a load resistance parallel to R_2 , the $V_{out} = V_{in} \frac{(R_2 // R_L)}{R_1 + (R_2 // R_L)}$

5.CIRCUIT DIAGRAM:

Circuit Diagram :

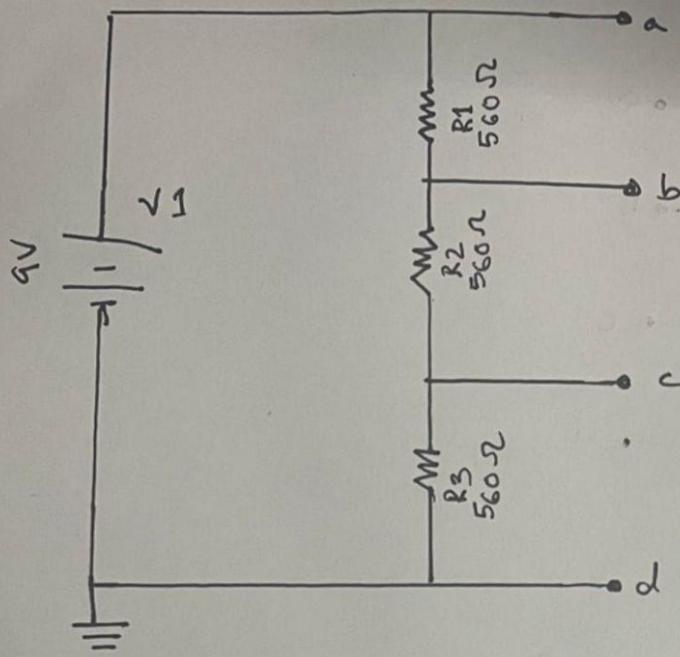

Circuit 1

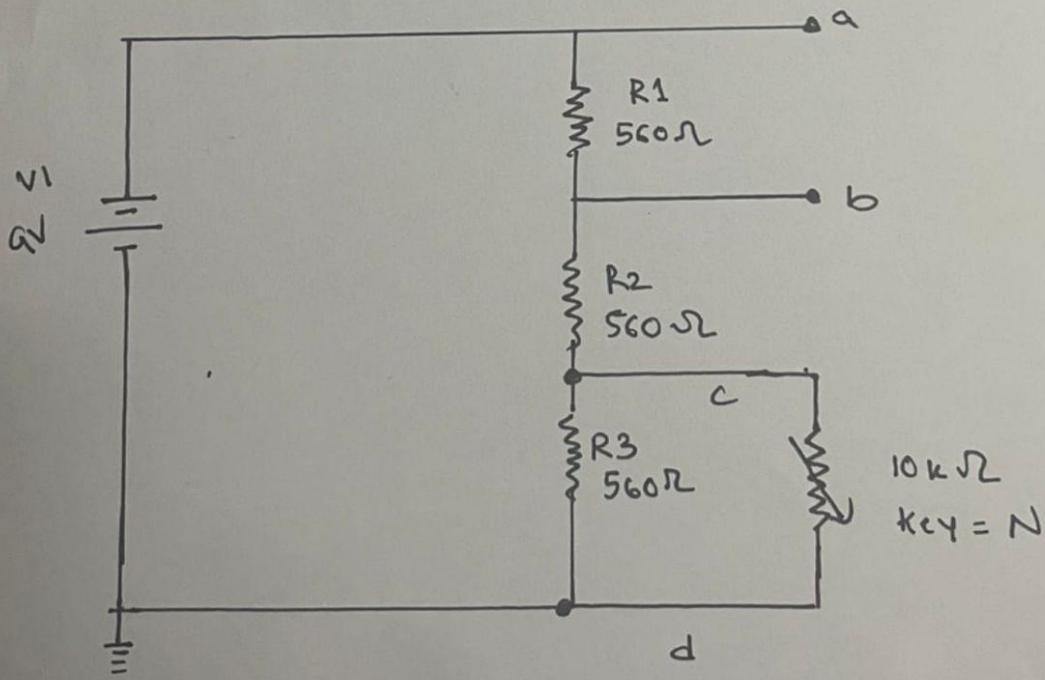

Circuit 2

6.RESULTS:

Zannatul Ferdous Ahma
1921171042

Data and Table :

	Circuit 1	Circuit 2 (R ₄ = 1kΩ)	Circuit 2 (R ₄ = 4kΩ)	Circuit 2 R ₄ = 7kΩ	Circuit 2. R ₄ = 10kΩ.
R _T	1.680kΩ	1.205kΩ	1.635kΩ	1.623kΩ	1.66kΩ.
E	9V	9V	9V	9V	9V
I	5.367mA	7.47mA	5.864mA	5.547mA	5.454mA.
V _{R1}	3V	4.183V	3.284V	3.106V	3.054V
V _{R2}	3V	4.183V	3.284V	3.106V	3.054V
V _{R3}	3V.	6.33.80mV	2.432V	2.788V	2.892V.
I _{R1}	5.367mA	7.47mA	5.864mA	5.547mA	5.464mA
I _{R2}	5.367mA	7.47mA	5.864mA	5.547mA	5.454mA.
I _{R3}	5.367mA 5.367mA	4.344mA 1.192mA	4.344mA	4.978mA	5.164mA.

Table C.1 .

Table 1:

RL.	V _{out} (measured)	V _{out} (calculated)	% Error
0	3V.	3V	0%
1k	633.80mV	2.184	-10.97%
4k	2.432V	2.744	11.38%
7k	2.788V	2.848	2.11%
10k	2.892V	2.892	0%

Calculations:

$$\text{for } 0\text{k}\Omega \\
 R_p = (560 + 560 + 560)\Omega \\
 = 1680\Omega.$$

$$V = 9V. \\
 I = \frac{V}{R_p} = \frac{9}{1680} = 5.357mA.$$

$$\text{so, } V_{out} = IR_3 \\
 = 5.357mA \times 560\Omega \\
 = 3V.$$

$$V_{out}(\text{measured}) = 3V.$$

$$\text{so, \% Error} = \frac{3-3}{3} = 0\%$$

For 1KΩ

$$R_P' = \left(\frac{1}{R_3} + \frac{1}{R_4} \right)^{-1} = \left(\frac{1}{1000} + \frac{1}{560} \right)^{-1} = 358.974 \Omega.$$

$$R_P^T = (560 + 560 + 358.974) \Omega \\ = 1478.974 \Omega.$$

$$\text{So, } I_1 = \frac{9}{1478.974} = 6.085 \text{ mA.}$$

$$V_{\text{out (real)}} = 358.974 \times 6.085 \text{ mA} \\ = 2.184 \text{ V.} \quad | \quad \% \text{ Error} = \frac{2.184 - 0.6338}{2.184} \\ V(\text{measured}) = 0.6338 \quad = 70.97\%$$

For 4KΩ

$$R_P' = \left(\frac{1}{4000} + \frac{1}{560} \right)^{-1} = 491.2280 \Omega.$$

$$R_P^T = 1611.22 \Omega.$$

$$I_2 = 5.5858 \times 10^{-3} \text{ A.}$$

$$V_{\text{out}} = I_2 R_P' \\ = 2.744 \text{ V.}$$

$$V(\text{mea}) = 2.432 \text{ V.}$$

$$\% \text{ error} = \frac{2.432 - 2.744}{2.432} \times 100$$

$$\% \text{ Error} = \frac{2.74 - 2.432}{2.74} \times 100 \\ = 11.38\%$$

7.DISCUSIONS:

7) Discussion :

The name of our experiment is loading effect of voltage dividers circuit. In this experiment we learned to analyze the voltage dividers circuit behaves when there is no load resistance connected. As well as we learned how to evaluate the performance of voltage divider circuit due to loading. In this experiment we can notice that here V_{out} (measured) and V_{out} (calculated) are nearly identical. Since we used a simulator for the circuits, for that we got nearly closed values. There was not much differences between theoretical and practical results. Also when we increased resistance, we saw the voltage is increasing too. But at one point the voltage became constant. Here we got percentage errors but the percentage would be higher if we do this practically.

8. QUESTIONS:

Khalid Hasan Prodhan
1812188642

Question/Answer:

1. As the resistance of the loading effect resistors is increased, the volt increases. This is because the R_3 (the load resistor) is in parallel with the R_2 resistor and their combinational resistor is lower than the individual resistor of R_2 and R_3 . This cause the current flow across these parallel resistors to be more and the voltage drop across the combined resistance increases. Hence, V_{out} is more as the load resistance is increasing. Now let's look at the issue mathematically, when the load resistance is $1k\Omega / 1000\Omega$, the combined resistance is 850.974Ω and for

that v_{out} is found to be 3.906 V.
when the load resistance is $4\text{k}\Omega / 4000\Omega$ then the combined resistance
is 491.228Ω and for that v_{out}
is found to be 4.673 V. when the
load resistance is $7\text{k}\Omega / 7000\Omega$
then the combined resistance is
 518.519Ω and v_{out} found to be
4.808 V. when the load resistance
is $10\text{k}\Omega / 10000\Omega$, the combined
resistance is 530.303Ω and for
that v_{out} is found to be 4.864 V.
so, we can conclude as the

load resistance value increases, the value of the combined resistance increases, the value of v_{out} also increases.

2 Theoretical value of v_{out} for no load resistance is :

$$\begin{aligned} v_{out} &= \left\{ \left(v_{in} * R_2 \right) / \left(R_1 + R_L \right) \right\} v \\ &= \left\{ \left(10 * 560 \right) / \left(560 + 560 \right) \right\} v \\ &= 5.000 \text{ V} \end{aligned}$$

$$R_T = (R_L || R_3) = \left\{ (R_2 * R_3) / (R_L + R_3) \right\}$$

Theoretical value of V_{out} for 1k load resistor is :

$$\text{when } R_3 = 1K = 1 \times 10^3 \Omega = 1000 \Omega$$

$$R_T = \left\{ (560 \times 1000) / (560 + 1000) \right\} \Omega \\ = 358.974 \Omega$$

$$V_{out} = \left\{ V_{in} \times (R_2 || R_3) \right\} / (R_1 + (R_2 + R_3)) \\ = \left\{ (10 \times 358.974) / (560 + 358.974) \right\} V \\ = 3.906 V$$

Theoretical value of V_{out} for 4k load resistor is :

$$\text{when } R_3 = 4K = 4 \times 10^3 \Omega = 4000 \Omega$$

$$R_T = \left\{ \left(560 \times 4000 \right) / (560 + 4000) \right\} \Omega$$
$$= 491.228 \Omega$$

$$V_{out} = \left\{ \left(10 \times 491.228 \right) / (560 + 491.228) \right\} V$$
$$= 4.67289 V$$
$$\approx 4.673 V$$

Theoretical value of V_{out} for $7k$ load
resistor is

$$\text{when } R_L = 7k = 7 \times 10^3 \Omega = 7000 \Omega$$

$$R_T = \left\{ \left(560 + 7000 \right) / (560 + 7000) \right\} \Omega$$
$$= 518.5185 \Omega$$
$$\approx 518.519 \Omega$$

$$V_{out} = \left\{ \left(10 \times 518.519 \right) / (560 + 518.519) \right\} V$$

$$= 4.80769 V$$

$$\approx 4.8088 V$$

Theoretical value of V_{out} for
10k load resistor as :

$$\text{when } R_3 = 10k = 10 \times 10^3 \Omega = 10000 \Omega$$

$$R_T = \left\{ (560 + 10000) / (560 + 10000) \right\} \Omega \\ = 530.303 \Omega$$

$$V_{out} = \left\{ (10 \times 530.303) / (660 + 530.303) \right\} V$$

$$= 4.86381 V$$

$$\approx 4.864 V$$

3. We perform this part by multism
(a circuit analysis tool that allows the user to simulate a circuit and extract key voltages and current). This is how, we performed this part successfully.

Experimental value of V_{out} for no load resistors : $V_{out} = 5.000 \text{ V}$

Experimental value of V_{out} for $1k$ load resistor is $V_{out} = 5.000 \text{ V}$

Experimental value of V_{out} for $1k$ load resistor $V_{out} = 3.906 \text{ V}$

Experimental value of V_{out} for $4k$

load resistor is $V_{out} = 4.673V$

Experimental value of V_{out} for

$7k$ load resistor as, $V_{out} = 4.808V$

Experimental value of V_{out} for $10k$

load resistor is : $V_{out} = 4.864V$

From the Question 2,

theoretical value of V_{out}

For No load resistor is $= 5.000V$

" $5k$ " " " " $= 3.906V$

" $4k$ " " " " $= 4.673V$

" $7k$ " " " " $= 4.808V$

7. Error for V_{out} for no load resistor

$$= \{(5-5)/5\} \times 100\%$$

$$= 0.00\%$$

8. Error for V_{out} for 1k load resistor

$$= \{(3.906 - 3.966)/3.906\} \times 100$$

$$= 0.00\%$$

9. Error for V_{out} for 4k load resistor

$$= \{(4.673 - 4.673)/4.673\} \times 100$$

$$= 0.00\%$$

10. Error for V_{out} with 7k load resistor

$$= \{(4.808 - 4.808)/4.808\} \times 100$$

$$= 0.00\%$$


% Error of V_{out} for $10k$ load -

$$\text{resistor} = \{(4.864 - 4.864) / 4.864\} \times 100 \\ = 0.00\%$$

It is seen that the theoretical values of V_{out} for each resistor are very close or accurate as the experimental values. So, we can conclude that the loading effect of a circuit supports the theory -

4. Loading effect can be defined as the effect on the source by the load impedance. Usually a loading effect reduces the voltage level of a voltage sources. When load current increases, the voltage drop across intend impedance (resistance in circuit) increases. That is why the lesser output voltage available at terminals. In that case, whenever a load is connected to any device or machine then it draws more current before and when current increase than the voltage decrease.

Attachments:

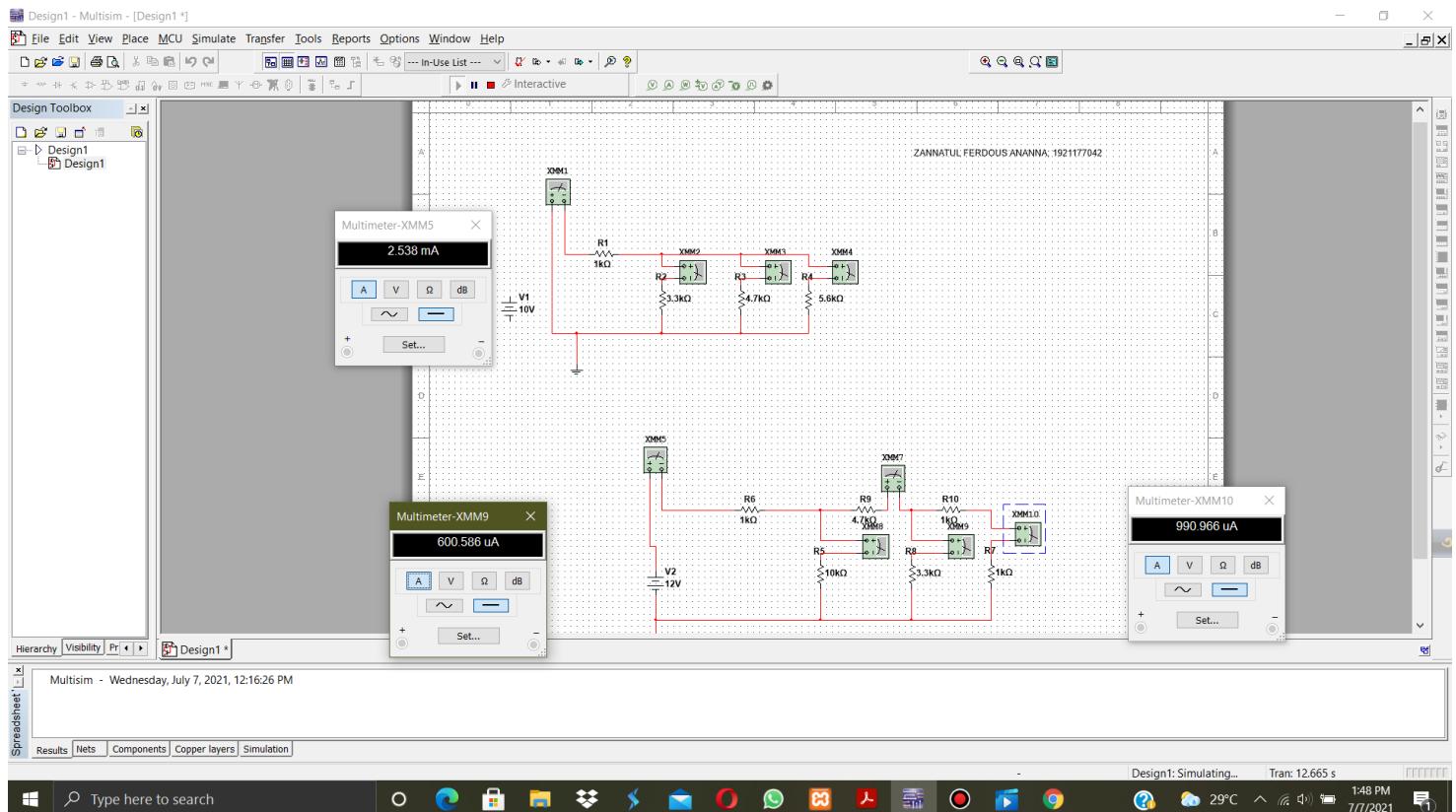

Contributions :

1.	Khalid Hasan Prodhan	8(Question & Answer)
2.	Zannatul Ferdous Ananna	4,6(Theory & Result)
3.	Nazmoon Nahar Punom	7(Discussion)
4.	Parinda Rahman	1,2,3,5>Title, Objective,Circuit Diagram)

Reference :

1. <https://learn.sparkfun.com/tutorials/voltage-dividers/all?fbclid=IwAR3N1H1wfdcnVz3OufLEqEihTwX3V3yo7ClqoLFXJBf5EZVVxh3N2XFjx34>